Communication

MIAT-C3X FPGA Development Board

■浯陽科技有限公司





Outline

- ☐ Part I
 - Design Consideration
 - Buadrate Generator
 - Transmitter
- ☐ Part II
 - Receiver
- Part III
 - Time for Questions
- Part IV
 - Project Architecture
 - QuartusII Setting




Part - I

UART TRANSMITTER DESIGN



Transmitter - UART Communication Protocol

□ UART Transmitter Protocol - Waveform

 


- Transmit form the last bit of the byte
 - 0x55(01010101₂)



Transmitter - Design Consideration

☐ Timing Diagram

 


- ☐ Describe TX **behavior**
 - Serially, shift 10 bits
 - Hold a bit during a period

Buadrate _*	One Packet+	One Bit↓	
	Transmission Time	Transmission Time∘	
1200 bps	8330 us#	833 us-	
2400 bps₽	4160 us₽	416 us.	
4800 bps₽	2080 us₽	208 us₽	
9600 bps₽	1040 us₽	104 us₊	
19200 bps₽	520 us₽	52 us₽	
38400 bps₽	260 us₽	26 us₽	
57600 bps₽	170 us∘	17 us₽	
115200 bps₽	80 us₽	8 us&	




Transmitter – Design Entity

Timing Diagram

 

 
- Output work signal
- Serial to Parallel Converter Module
 - Shift bit






Buadrate Gen. – Design Entity



 


☐ RTL Viewer

 



Exercise I – Buadrate Generator

- Design a Buadrate Generator Module
 - Generate a reference signal can be programmed period
- ☐ Simulate Result

 



Exercise I – Buadrate Generator, Cont.

Counter Bit Width

32-bit Timing analyzer report


Timing Analyzer Summary							
	Туре	Slack	Required Time	Actual Time	9	From	То
1	Worst-case tsu	N/A	None	7.844 ns		tbr_i_buadrate_width[4]	r_cnt[0]
2	Worst-case tco	N/A	None	6.872 ns		r_btx	tbr_o_buadrate_tx
3	Worst-case th	N/A	None	0.138 ns		tbr_i_enable	r_btx
4	Clock Setup: 'tbr_i_clock'	N/A	None	147.51 MHz	(period = 6.779 ns)	r_cnt[0]	r_cnt[0]
5	Total number of failed paths						

8-bit Timing analyzer report

Timing Analyzer Summary							
	Туре	Slack	Required Time	Actual Time		From	То
1	Worst-case tsu	N/A	None	5.188 ns		tbr_i_buadrate_width[2]	r_cnt[0]
2	Worst-case tco	N/A	None	7.959 ns	V	r_btx	tbr_o_buadrate_tx
3	Worst-case th	N/A	None	0.559 ns		tbr_i_enable	r_btx
4	Clock Setup: 'tbr_i_clock'	N/A	None	243.66 MHz (per	iod = 4.104 ns)	r_cnt[0]	r_cnt[0]
5	Total number of failed paths						



PS Converter – Design Entity

 



PS Converter – Synthesis Report

☐ Timing Report

Tir	Timing Analyzer Summary					
	Туре	Slack	Required Time	Actual Time	From	То
1	Worst-case tsu	N/A	None	3.101 ns	tx_i_writedata[2]	r_payload[3]
2	Worst-case tco	N/A	None	8.288 ns	r_payload[0]	tx_o_tx
3	Worst-case th	N/A	None	0.969 ns	tx_i_writedata[0]	r_payload[1]
4	Clock Setup: 'tx_i_clock'	N/A	None	Restricted to 250.00 MHz (period = 4.000 ns)	m_state[0]	r_payload[7]
5	Total number of failed paths					


☐ Synthesis Report

· ·	
Flow Summary	
Flow Status	Successful - Fri Jul 16 20:28:04 2010
Quartus II Version	10.0 Build 218 06/27/2010 SJ Full Version
Revision Name	miatc3x
Top-level Entity Name	transmitter
Family	Cyclone III
Device	EP3C25F256C8
Timing Models	Final
Met timing requirements	Yes
Total logic elements	18 / 24,624 (< 1 %)
Total combinational functions	18 / 24,624 (< 1 %)
Dedicated logic registers	16 / 24,624 (< 1 %)
Total registers	16
Total pins	13 / 157 (8 %)
Total virtual pins	0
Total memory bits	0 / 608,256 (0 %)
Embedded Multiplier 9-bit elements	0 / 132 (0 %)
Total PLLs	0 / 4 (0 %)



Exercise II – PS Converter


- Design a Parallel to Serial Converter
 - A shift controller
- ☐ Simulate

 



Exercise III - Serial Transmitter


- Integrate Modules
 - Buadrate Generator
 - Parallel to Serial Converter
 - Use the reference signal to trigger the PX Converter

 



Exercise III - Serial Transmitter

☐ Simulate

 


☐ Issue

Warning: Found 1 node(s) in clock paths which may be acting as ripple and/or gated clocks
-- node(s) analyzed as buffer(s) resulting in clock skew

Info: Detected ripple clock "tx_buadrate:tbr_0|r_btx" as buffer




Modified Serial Transmitter

 




 Exercise VI – Modified Serial Transmitter

- ☐ Modified ripple clock issue
 - Modified reference signal approach
- ☐ Simulate



☐ RTL Viewer

 


[Project Name] /uart_para1



 Exercise V – Porting Serial Transmitter

- Porting Serial Transmitter to MIATC3X Board
 - Reset synchronous issue
 - IO mapping
 - Top controller




PC Client



[Project Name] /uart_para2



MIATC3X Board PIN MAPPING

 




Part - II

UART RECEIVER DESIGN



UART Communication Protocol – Receiver

□ UART Receiver Protocol

 


- ☐ Rx Signal
 - Wait Start Bit
 - Fetch Data Bit
 - Detect Stop Bit



Receiver - Design Consideration

□ UART Receiver Protocol

 


- ☐ Detect RX Bit
 - Signal phase shift
 - Error stop bit




Receiver - Design Consideration, Cont.

☐ Timing Diagram

 

 
- Buadrate Generator
 - Over Sampling
 - Phase Shift
 - Programmable
- ☐ SP Converter
 - Fetch Data Bit





Receiver – Design Entity


Behavior

 



Exercise VI – Serial Receiver


- Design Serial Receiver
 - Reuse Buadrate Generator
 - Implement Serial to Parallel Converter

 



Exercise VI – Serial Receiver, Cont.


☐ Simulate

 



Exercise VII – Receiver and Transmitter


- Receive and transmit
 - Receive a value
 - Return it +1

 



 Exercise VII – Receiver and Transmitter, Cont.

- ☐ Monitor internal signal
 - SignalTapII



Client





Part - III

TIME FOR QUESTION



Note:




Part - IV

APPENDIX




Project Architecture

 




Quartus II Project Setting

 



Quartus II Project Setting, Cont.

 



Quartus II Project Setting, Cont.

